

Intro To Static Timing Analysis




UNIVERSITY OF MINNESOTA

Driven to DiscoverSM

Introduction

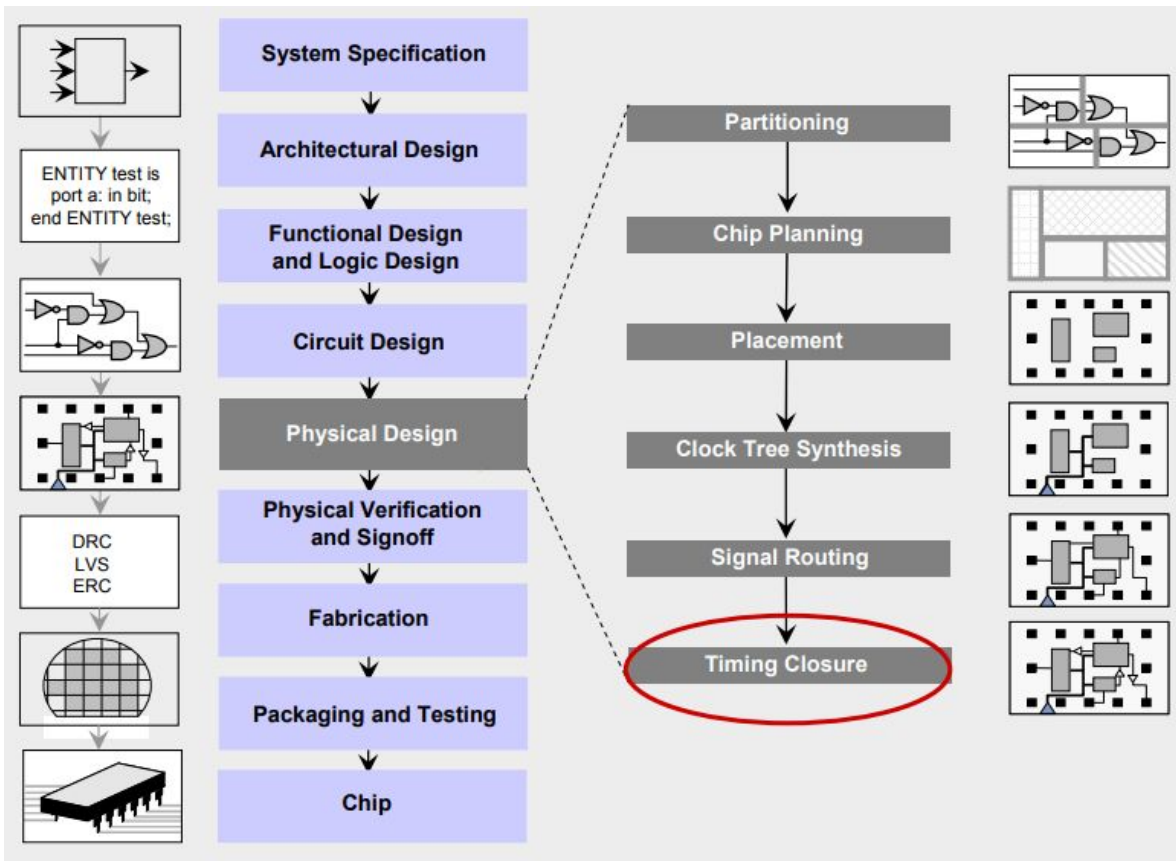- FPGA Flow and ASIC Design Flow share a lot of similar processes



Timing Closure


- Timing closure is the process of satisfying timing constraints through design and netlist modifications
- Designers should achieve Timing Closure
 - Style of Digital System Design
 - Optimization process that meet timing constraints (This is automated, so designer doesn't have control of this)
 - This is where design automation engineers play their role
 - Optimizations occur at Partitioning, Placement, and Routing
 - Timing-Driven Implementations minimizes Signal Delays



UNIVERSITY OF MINNESOTA

Driven to DiscoverSM

Example

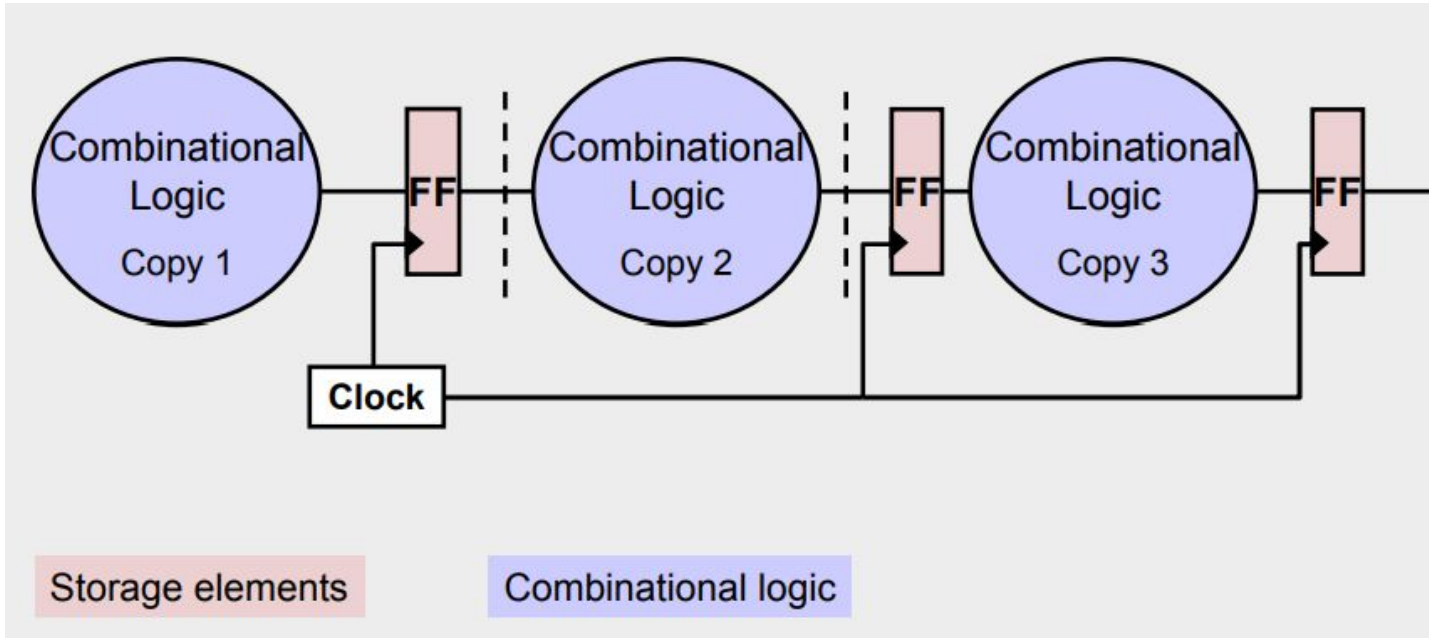


Static Timing Analysis

- Main delay concerns in sequential circuits
 - **Gate delays** are due to gate transitions
 - **Wire delays** are due to signal propagation along wires
 - **Clock skew** is due to the difference in time the sequential elements activate




Terminologies

 - **Setup Time** - the time the data has to arrive before the clock to ensure correct sampling.



Terminologies

 - **Hold Time** -the time the data has to be stable after the clock to ensure correct sampling.




Terminologies

- **Required Time (R_t)** - represents the time by which data has to be present at that node
 - Determined by the Clock Frequency
- **Arrival Time (A_t)** - represents the time at which the data arrives at the
 - Determined by Wire Delay and Gate Delay
- **Setup Slack = $R_t - A_t$**
 - Commonly called as Slack
- **Hold Slack = $A_t - R_t$**



 
Example - Arrival Time

- Assumptions:
 - All inputs arrive at time 0
 - All gate delays = 1
 - All wire delays = 0
- Question: Arrival time of each gate? Circuit delay?



 
Example - Arrival Time

- Assumptions:
 - All inputs arrive at time 0
 - All gate delays = 1
 - All wire delays = 0
- Question: Arrival time of each gate? Circuit delay?



 
Example - Required Time

- Assumptions:
 - All inputs arrive at time 0
 - All gate delays = 1, wire delay = 0
 - Clock period = 7
- Question: maximum required time (RT) of each gate? (i.e., if the gate output is generated later than RT, clk period is violated)



 
Example - Required Time

- Assumptions:
 - All inputs arrive at time 0
 - All gate delays = 1, wire delay = 0
 - Clock period = 7
- Question: maximum required time (RT) of each gate? (i.e., if the gate output is generated later than RT, clk period is violated)



 
Example - Slack

- Assumptions:
 - All inputs arrive at time 0
 - All gate delays = 1, wire delay = 0
 - Clock period = 7
- Question: What is the maximum amount of delay each gate can be slower not to violate timing?



 Example - Slack

- Assumptions:
 - All inputs arrive at time 0
 - All gate delays = 1, wire delay = 0
 - Clock period = 7
- Question: What is the maximum amount of delay each gate can be slower not to violate timing?



Implications

- **Negative slack** at any output means the circuit does not meet timing
- **Positive slack** at all outputs means the circuit meets timing

Setup	Hold	Pulse Width
Worst Negative Slack (WNS): 5.631 ns	Worst Hold Slack (WHS): 0.116 ns	Worst Pulse Width Slack (WPWS): 4.500 ns
Total Negative Slack (TNS): 0.000 ns	Total Hold Slack (THS): 0.000 ns	Total Pulse Width Negative Slack (TPWS): 0.000 ns
Number of Failing Endpoints: 0	Number of Failing Endpoints: 0	Number of Failing Endpoints: 0
Total Number of Endpoints: 43	Total Number of Endpoints: 43	Total Number of Endpoints: 23


All user specified timing constraints are met.



How to Achieve Timing Closure?

- Timing Corrections Include

 - Gate Sizing
- Buffer Insertion
- Netlist Re-Construction
 - Cloning: duplicating gates
 - **Redesign** of fanin or fanout tree: changing the topology of gates
 - Swapping communicative pins: changing the connections
 - Gate decomposition: e.g., changing AND-OR to NAND-NAND
 - Boolean restructuring: e.g., applying Boolean laws to change circuit gates



END

Any Questions?

